

1 Logic Gates

Logic gates perform logical operations that take binary input (0's and 1's) and produce a single binary output. They are used in most electronic devices including:

Table 1: Logic Gates

Smartphones	Tablets	Memory Device
		